

ETI SUPPLEMENT

555 TIMER APPLICATIONS

DESCRIBED BY
R. M. MARSTON

THE 555 TIMER is a highly versatile low-cost IC that is specifically designed for precision timing applications, but which can also be used in a variety of monostable multi-vibrator, astable multivibrator, and Schmitt trigger applications. The device was originally introduced by Signetics, but is now available under the '555' designation from many other manufacturers.

The 555 has many attractive features. It can operate from supply voltage in the range 4.5V to 16V. Its output can source (supply) or sink (absorb) any load current up to a maximum of 200mA, and so can directly drive loads such as relays, LED's, low-power lamps, and high impedance speakers. When used in the 'timing' mode, the IC can readily produce accurate timing periods that can be varied from a few microseconds to several hundred seconds via a single R-C network. Timing periods are virtually independent of actual supply rail voltage, have a temperature coefficient of only .005% per °C, can be started via a TRIGGER command signal, and can be aborted by a RESET command signal.

When used in the monostable mode, the IC produces output pulses with typical rise and fall times of a mere 100nS. It can be made to produce pulse-width modulated (PWM) pulses in this mode by feeding fixed frequency clock pulses to the TRIGGER terminal and, by feeding the modulation signal to the CONTROL VOLTAGE terminal.

When used in the astable mode both the frequency and the duty cycle of the waveform can be accurately controlled with two external resistors and one capacitor. The output signals can be subjected to frequency sweep control, frequency modulation (FM), or pulse-position modulation (PPM) by applying suitable modulation signals to the CONTROL VOLTAGE terminal of the IC.

THE 555: HOW IT WORKS

The 555 is available under a variety of specific type numbers but is generally referred to simply as a '555 timer.' The device is available in a number of packaging styles, including 8 and 14-pin dual-in-line (DIL) and 8-pin TO-99 types. Throughout this article all circuits are designed around the standard 8-pin DIL versions of the device.

Fig 1 shows the outline and pin notations of the standard 8-pin DIL version of the 555, and Fig 2 shows

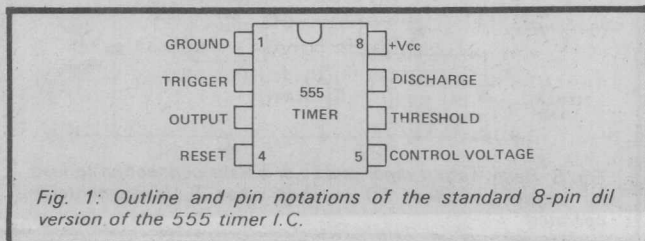


Fig. 1: Outline and pin notations of the standard 8-pin dill version of the 555 timer I.C.

the functional block diagram of the same device (within the double lines), together with the connections for using it as a basic monostable generator. The following explanation of device operation assumes that the 555 is used in the monostable configuration shown in Fig 2.

The 555 houses 2 diodes, 15 resistors, and 23 transistors. These components are arranged in the form of one voltage-reference potential divider, two voltage-comparator op-amps, one R-S flip-flop, a low-power complementary output stage, and a slave transistor. The voltage-reference potential divider comprises three 5kΩ resistors in series, and is connected across the supply lines. Consequently, $2/3 V_{cc}$ appears at the junction of the upper two resistors of

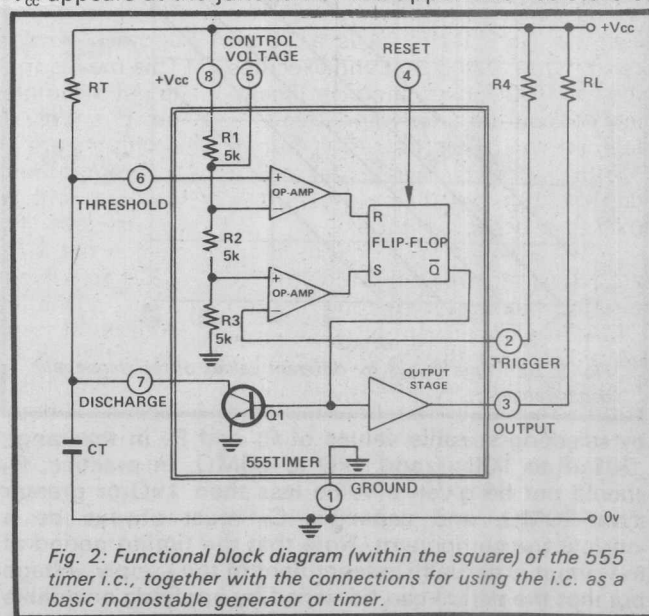


Fig. 2: Functional block diagram (within the square) of the 555 timer i.c., together with the connections for using the i.c. as a basic monostable generator or timer.

the potential divider, and is fed to one input terminal of the upper voltage-comparator op-amp and $1/3 V_{cc}$ appears at the junction of the two lower resistors of the potential divider, and is fed to one input terminal of the lower voltage-comparator op-amp. The outputs of the two comparators control the R-S flip-flop, which in turn controls the states of the complementary output stage and the slave transistor. The state of the flip-flop can also be influenced by signals applied to the pin 4 RESET terminal.

When the monostable or timing circuit of Fig 2 is in its quiescent state the pin 2 TRIGGER terminal of the chip is held high via R1. Under this condition Q1 is driven to saturation and forms a short circuit across external timing capacitor C_T , and the pin 3 output terminal of the IC is driven to the low state. The monostable action can be initiated by applying a negative-going trigger pulse to pin 2. As this pulse falls

555 TIMER APPLICATIONS


below the $1/3 V_{cc}$ reference value of the built-in potential divider the output of the lower voltage comparator op-amp changes state and causes the R-S flip-flop to switch over. As the flip-flop switches over it cuts off Q1 and drives the pin 3 output of the chip to the high state.

As Q1 cuts off it removes the short from timing capacitor C_T , so C_T starts to charge exponentially towards the supply rail voltage until eventually the voltage across C_T reaches $2/3 V_{cc}$. At this point the upper voltage comparator op-amp changes state and switches the R-S flip-flop back to its original condition, so Q1 turns on, rapidly discharging C_T , and simultaneously the pin 3 output of the IC reverts to its low state. The monostable operating sequence is then complete. Note that, once triggered, the circuit cannot respond to additional triggering until the timing sequence is complete, but that the sequence can be aborted at any time by feeding a negative-going pulse to pin 4.

The delay time of the circuit, in which the pin 3 output is high, is given as

$$t = 1.1 R_T C_T$$

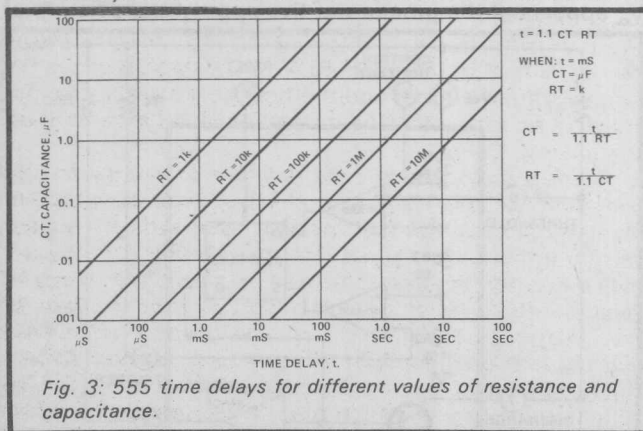where $t = \text{mS}$, $R_T = \text{k}\Omega$, and $C_T = \mu\text{F}$. Fig 3 shows how delays from $10 \mu\text{s}$ to 100 seconds can be obtained



by selecting suitable values of C_T and R_T in the range $0.001 \mu\text{F}$ to $100 \mu\text{F}$ and $1 \text{k}\Omega$ to $10 \text{M}\Omega$. In practice, R_T should not be given a value less than $1 \text{k}\Omega$ or greater than $20 \text{M}\Omega$, and capacitor C_T must always be a low-leakage component. Note that the timing period of the circuit is virtually independent of the supply voltage but that the period can be varied by applying a variable resistance or voltage between the ground and pin 5 CONTROL VOLTAGE terminals of the chip. This facility enables the periods to be externally modulated or compensated.


The pin 3 output terminal of the IC is normally low, but switches high during the active monostable sequence. The output can either source or sink currents up to a maximum of 200mA , so external loads can be connected between pin 3 and either the positive supply rail or the ground rail, depending on the type of load operation that is required. The output switching rise and fall times are typically about 100 nanoseconds. Having cleared up these points, let's now go on and look at some practical applications of the 555 timer I.C.

50 SECOND TIMER

This 50 second timer or pulse generator gives a direct voltage output at pin 3 which is normally low, but goes

high for the duration of the timing period. Optional components R_4 and LED (shown dotted) give a visual indication of the timer action. The circuit works in the same basic way as already described, except that the timing action is initiated by momentarily shorting pin 2 to ground via START switch S_1 . Note from the circuit waveforms that a fixed-period output pulse is available at pin 3 and an exponential sawtooth with an identical period is available at pin 7: The sawtooth waveform has a high output impedance.

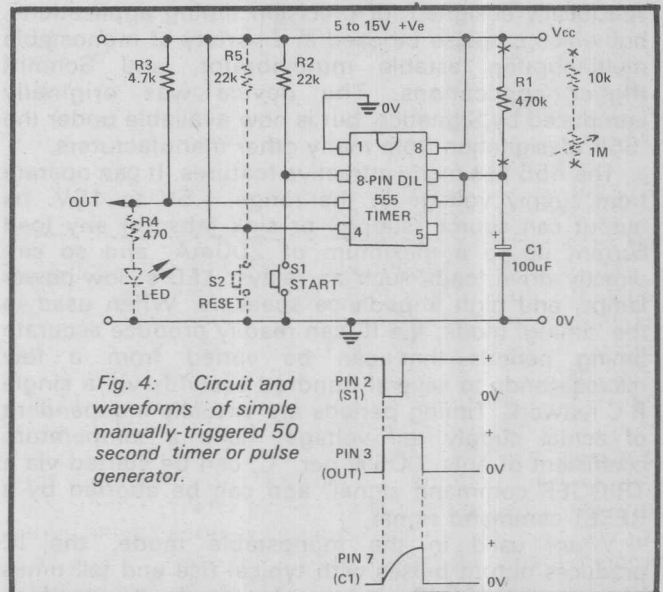
The basic timer circuit of Fig 4 can be varied in a number of ways. The timing period can be made variable between approximately 1.1 seconds and 110 seconds by replacing R_1 with a $10 \text{k}\Omega$ fixed resistor and a $1 \text{M}\Omega$ variable resistor in series.



The period can be further varied, if required, by switch-selecting decade values of timing capacitance. The dotted section shows how the circuit can be provided with a RESET facility, so that a timing period can be aborted at any time, by taking pin 4 to the positive supply rail via resistor R_5 and wiring RESET switch S_2 between pin 4 and ground.

The timing circuit of Fig 4 can be used to drive non-inductive loads at currents up to 200mA directly. They can be used to drive inductive relay loads by using the basic connections shown in Fig 5.

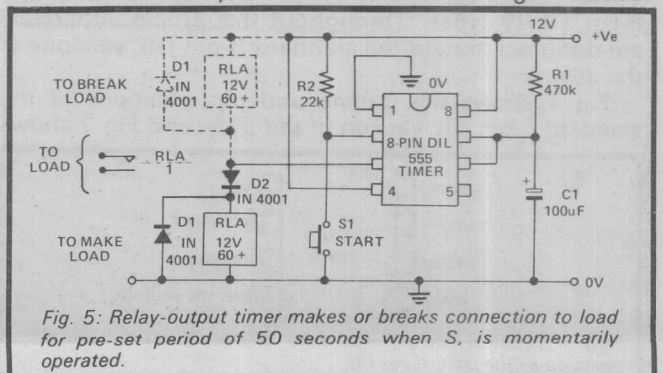The Fig 5 circuit is designed to apply a connection to a normally-off external load for a pre-set period of 50 seconds when START switch S_1 is momentarily closed. The relay is normally off, but turns on for the 50 second period when the timing cycle is initiated. D_2 is wired in series with the relay coil to counteract the slight residual



voltage that appears at pin 3 of the IC under the OFF condition and thus ensure that the relay turns fully off. The dotted section shows how this circuit can be used to switch off a normally-on load.

Note in Fig 5 and all other relay-output circuits described here, that the relays used can be any 12 volt types that draw ON currents of less than 200mA, e.g., that have coil resistances greater than 60Ω.

The basic relay-driving timer circuit of Fig 5 can be adapted for use in a variety of useful applications. Some typical examples are shown in Figs 6 to 9.

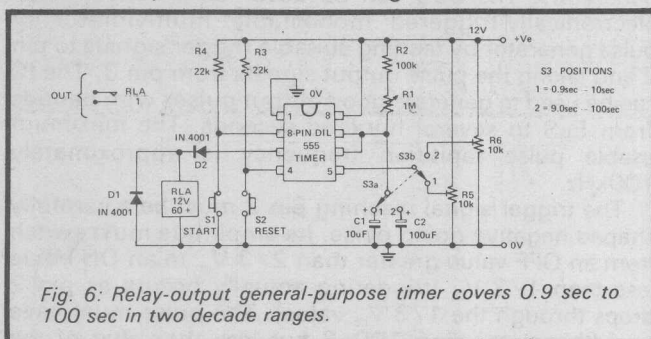


Fig. 6: Relay-output general-purpose timer covers 0.9 sec to 100 sec in two decade ranges.

Fig 6 shows the practical circuit of a relay-output general-purpose timer that covers 0.9 seconds to 100 seconds in two decade ranges: The circuit has a RESET facility provided via S_2 , so that timing periods can be aborted part way through a cycle if necessary. A noteworthy feature of this circuit is that the maximum timing periods of each decade range of the timer can be precisely pre-set via R_5 or R_6 , which effectively shunt the built-in potential divider of the 555 and thus influence the timing periods: This facility enables the circuit to give precise timing periods even when wide-tolerance timing capacitors are used.

To set up the Fig 6 circuit, first set R_1 to maximum value, set RANGE switch S_3 to position 1, activate START switch S_1 , and adjust R_5 to give a timing period of precisely 10 seconds. Next, set S_3 to position 2, activate START switch S_1 , and adjust R_6 to give a timing period of precisely 100 seconds. All adjustments are then complete, and the timer is ready for use.

DELAYED HEADLIGHT TURN-OFF

Fig 7 shows the practical circuit of an automatic delayed-turn-off headlight control system for automobiles. This facility enables the owner to use the car lights to illuminate his path for a pre-set time after parking as he leaves the garage or walks along a driveway, etc. The circuit does not interfere with normal headlight operation under actual driving conditions. It works as follows.

When the ignition switch is turned to the ON

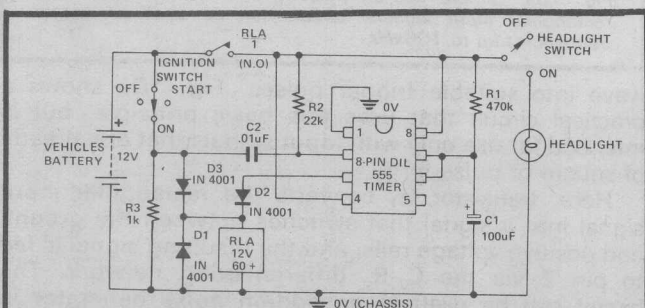


Fig. 7: Automatic delayed-turn-out headlight control system for automobiles.

position current is fed to the coil of the relay via D_3 and the 12 volt supply rail, so the relay turns on and contacts RLA/1 close. As the contacts close they connect the 12 volt supply to the timer circuit and to the headlight switch. Thus, under this 'ignition on' condition the headlights operate in the normal way. Note that, since one side of C_2 is connected directly to the positive supply rail and the other side is taken to the positive rail via R_2 , the capacitor is fully discharged under this condition.

The moment that the ignition switch is turned to the OFF position the D_3 -derived current supply to the relay coil is broken, and simultaneously a negative-going trigger pulse is fed to pin 2 of the 555 as the C_2 - R_3 junction drops to ground volts and C_2 charges up. Now, relays are inherently slow-acting devices, so contacts RLA/1 do not open instantaneously as the ignition switch is turned off. Conversely, the 555 is a very fast triggering device, and the instant that the trigger pulse is generated via the turn-off action of the ignition switch a timing cycle is initiated and current is fed to the relay coil via output pin 3 of the IC as it goes high. Thus the relay remains on for a pre-set period after the ignition switch is closed, and the positive supply rail remains connected to the headlight switch for the duration of this period. With the component values shown this period is roughly 50 seconds.

At the end of the 50 second timing period, pin 3 of the 555 switches to the low state and the relay turns off. As it does so, contacts RLA/1 open and remove the supply from the timer and the headlight switch, and the headlights turn off. The operating sequence is then complete.

Readers may care to note that the above system of operation is consistent with the practice adopted in many modern vehicles of feeding the headlight switch via the ignition switch, so that the headlights operate only when the ignition is turned on. On older types of vehicle, where headlight operation is independent of the ignition switch, a manually-triggered delayed-turn-off headlight or spotlight control facility can be obtained by using the circuit shown in Fig 8. The action of this circuit is such that, if the vehicle is parked with its lights off, they turn on for a pre-set 50 second period as soon as a push-button START switch is momentarily closed, and at the end of this period turn off again automatically.

The Fig 8 circuit uses a relay with two sets of normally-open relay contacts. The timing sequence is initiated by momentarily closing push-button switch S_1 . Normally, both S_1 and the relay contacts are open, so zero power is fed to the timer circuit and the lights are off. C_2 is discharged under this condition.

When S_1 is momentarily closed power is fed directly to the relay coil, and the relay turns on. As the relay

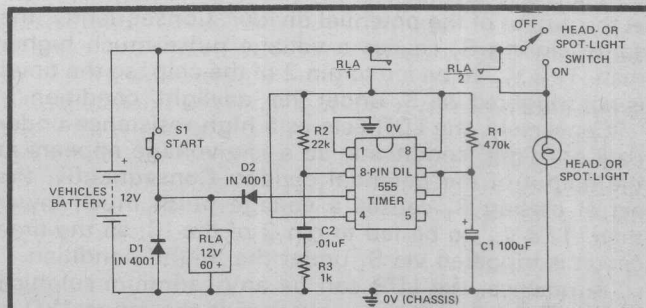


Fig. 8: Manually-triggered delayed-turn-off head- or spot-light control system for automobiles.

555 TIMER APPLICATIONS

turns on contacts RLA/2 close and apply power to the vehicle lights and contacts RLA/1 close and apply power to the timer circuit, but pin 2 of the IC is briefly tied to ground via C_2 and R_3 at this moment, so a negative trigger pulse is immediately fed to pin 2 and a timing cycle is initiated. Consequently, pin 3 of the 555 switches high at the moment that the relay contacts close, and thus locks the relay into the ON condition irrespective of the subsequent state of START switch S_1 , so the lights remain on for the duration of the 50 second timing cycle. At the end of the timing cycle pin 3 of the I.C. switches to the low state, so the relay turns off and contacts RLA/1 and RLA/2 open, disconnecting power from the timing circuit and the lights. The operating sequence is then complete.

PORCH LIGHT

Finally, to conclude this 'Timer Circuits' section of the 555 story, Fig 9 shows the circuit of a relay-output automatic porch light control unit that turns the porch lights on for a pre-set 50 second period only when suitably triggered at night time or under 'dark' conditions: The circuit is triggered via switch S_1 , which may take the form of a microswitch activated by a porch gate or a pressure-pad switch activated by body weight and concealed under a porch mat or rug.

The operation of the Fig 9 circuit relies on the fact that for correct timer operation the negative-going trigger pulse that is fed to pin 2 of the IC must fall below the internally-controlled ' $1/3 V_{cc}$ ' voltage value of the 555. If the trigger pulse does not fall below this value, timing cycles can not be initiated by the trigger signal.

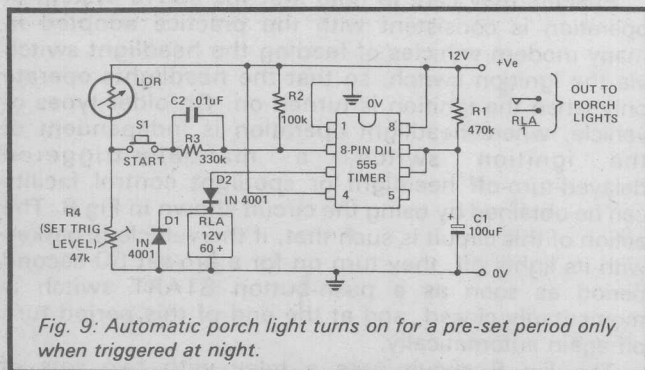


Fig. 9: Automatic porch light turns on for a pre-set period only when triggered at night.

In this design, light-dependent resistor LDR and preset resistor R_4 are wired in series as a light-dependent potential divider. One side of switch S_1 is taken to the output of this potential divider, and the other side of the switch is taken to pin 2 of the IC via the C_2 - R_3 combination. Under bright or daylight conditions the LDR acts as a low resistance, so a high voltage appears at the output of the potential divider. Consequently, the act of closing S_1 causes a voltage pulse much higher than ' $1/3 V_{cc}$ ' to be fed to pin 2 of the chip, so the timer is not triggered via S_1 under the 'daylight' condition.

Conversely, the LDR acts as a high resistance under dark or 'night' conditions, so a low voltage appears at the output of the potential divider. Consequently, the act of closing S_1 causes a voltage pulse much lower than ' $1/3 V_{cc}$ ' to be fed to pin 2 of the IC, so the time circuit is triggered via S_1 under the 'night' condition.

In practice, the LDR can be any cadmium-sulphide photocell that presents a resistance in the range $1k\Omega$ to $100k\Omega$ under the required minimum 'dark' turn-on condition, and R_4 can be adjusted to preset the

minimum 'dark' level at which the circuit will trigger. Note that the trigger signal is fed to pin 2 of the IC via the C_2 - R_3 combination, which act as a trigger signal conditioning network that effectively isolates the d.c. component of the LDR- R_4 potential divider from the trigger pin of the IC.

MONOSTABLE PULSE GENERATOR CIRCUITS

All the 555 timer circuits that we have looked at so far act essentially as monostable multivibrators or pulse generators. The 555 can be used as a conventional electronically-triggered monostable multivibrator or pulse generator by feeding suitable trigger signals to pin 2 and taking the pulse output signals from pin 3. The IC can be used to generate good output pulses with periods from $5\mu s$ to several hundred seconds. The maximum usable pulse repetition frequency is approximately 100kHz.

The trigger signal reaching pin 2 must be a carefully shaped negative-going pulse. Its amplitude must switch from an OFF value greater than $2/3 V_{cc}$ to an ON value less than $1/3 V_{cc}$ (triggering actually occurs as pin 2 drops through the $1/3 V_{cc}$ value). The pulse must have a width greater than 100ns but less than that of the desired output pulse, so that the trigger pulse is removed by the time the monostable period terminates.

One way of determining a suitable trigger signal for the 555 monostable circuit is to convert the input signal to a good square wave that switches between ground volts and the full positive supply rail voltage, and then couple this square wave to pin 2 of the IC via a simple short time-constant C-R differentiating network, which converts the leading or trailing edges of the square

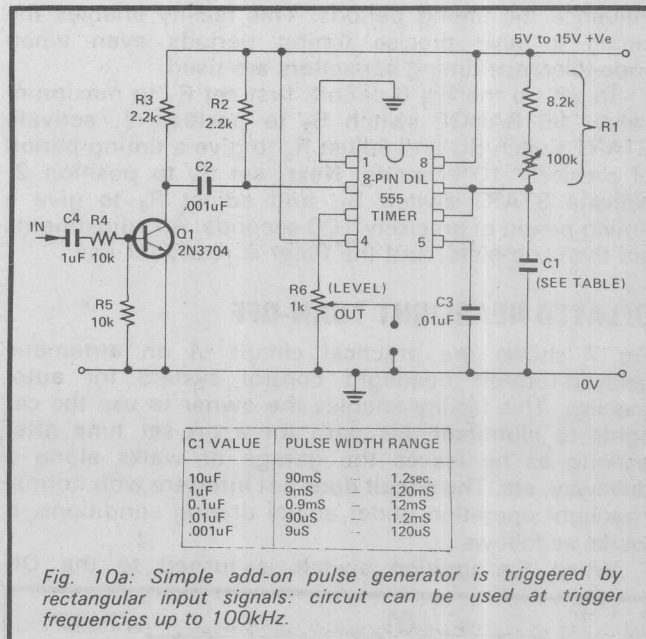


Fig. 10a: Simple add-on pulse generator is triggered by rectangular input signals: circuit can be used at trigger frequencies up to 100kHz.

wave into suitable trigger pulses. Fig. 10a shows a practical circuit that uses this basic principle, but is intended for use only with input signals that are already of square or pulse form.

Here, transistor Q_1 converts the rectangular input signal into a signal that switches between the ground and positive voltage rails, and the resulting signal is fed to pin 2 via the C_2 - R_2 differentiating network. The circuit can be used as an add-on pulse generator in conjunction with an existing square or pulse generator. Variable-amplitude output pulses are available from pin

Fig 10b shows how the above circuit can be modified so that it can be driven from any type of input waveform, including sine waves. Here, IC1 is connected as a simple Schmitt trigger, which converts all input signals into rectangular output signals, and these rectangular signals are used to drive the IC2 monostable circuit in the same way as described above. The Fig 10b circuit can thus be used as an add-on pulse generator in conjunction with an existing waveform generator of any type that produces output signals with peak-to-peak amplitudes greater than $1/2 V_{cc}$.

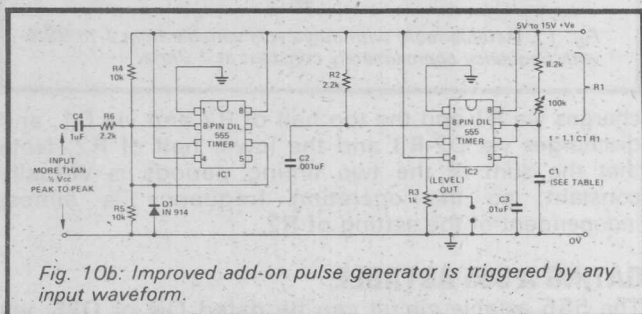


Fig. 10b: Improved add-on pulse generator is triggered by any input waveform.

Fig. 11: Add-on delayed pulse generator is triggered by any input waveform. For C_1 (and C_7) values, see table in Fig. 10a.

Fig. 11: Add-on delayed pulse generator is triggered by any input waveform. For $\bar{C}1$ (and $\bar{C}7$) values, see table in Fig. 10a.

Fig. 12: 3-stage sequential timer or pulse generator.

Finally, three or more monostable circuits can be connected, via C9, in a continuous loop, with the output of the last monostable feeding back to the input of the first monostable, to form a 'chaser' circuit in which the sequential action repeats to infinity. This type of circuit can be used to drive lamp or LED displays, etc. Note that the circuit is again provided with the S₂ SET facility, so that the circuit can be emptied at the moment that power is first applied.

Fig 13 shows the practical circuit of a basic 1kHz astable multivibrator, together with the formulas that define the timing of the circuit. Note that TRIGGER pin 2 of the chip is shorted to the pin 6 THRESHOLD terminal, and that timing resistor R2 is wired between pin 6 and DISCHARGE pin 7.

5V to 15V+ve

0V

8-PIN DIL 555 TIMER

OUT

R3 4.7k

R1 1k

R2 75k

C2 0.01uF

C1 0.01uF

0V

t_1

t_2

T

$t_1 = 0.693(R_1 + R_2)C_1$

$t_2 = 0.693(R_2)C_1$

$T = 0.693(R_1 + 2R_2)C_1$

$f = \frac{1.44}{(R_1 + 2R_2)C_1}$

IF R_2 IS GREATER THAN R_1 :

$t_1 \approx 0.7 R_2 C_1$

$t_2 \approx 0.7 R_2 C_1$

$T \approx 1.4 R_2 C_1$

$f \approx \frac{0.72}{R_2 C_1}$


Fig. 13: Basic circuit of 1KHz astable multivibrator, with timing formulas.

Fig. 13: Basic circuit of 1KHz astable multivibrator, with timing formulas.

Note in the above circuit that, if R2 is very large relative to R1, the operating frequency of the circuit is determined essentially by the R2 and C1 values, and that a virtually symmetrical output waveform is


555 TIMER APPLICATIONS

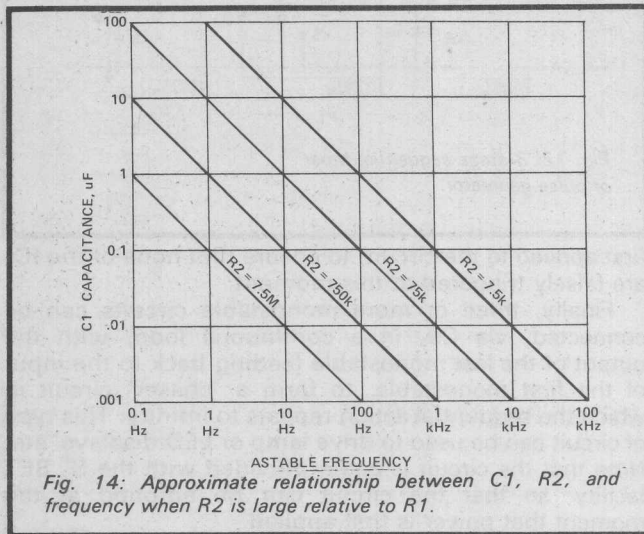generated. The graph of Fig 14 shows the approximate relationship between frequency and the C1-R2 values under the above condition. In practice, the R1 and R2 values of the circuit can be varied from 1k Ω up to tens of megohms. Note, however, that R1 has a significant




effect on the total current consumption of the circuit, since pin 7 of the IC is virtually grounded during half of the timing sequence. Also note that the duty cycle or mark/space ratio of the circuit can be pre-set at a non-symmetrical value, if required, by suitable choice of the R1 and R2 values.

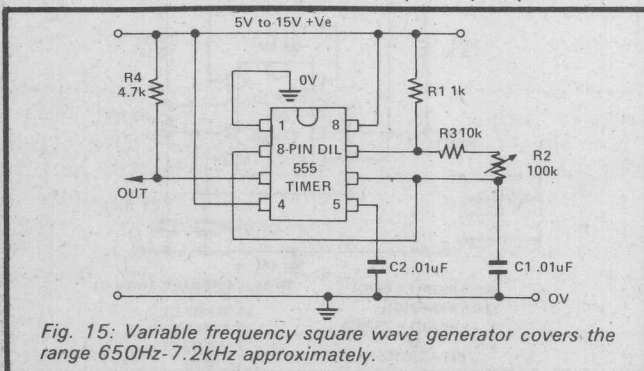The basic circuit of Fig 13 can be usefully modified in a number of ways. Fig 15, for example, shows how it can be made into a variable-frequency square wave




generator by replacing R2 with a fixed and variable resistor in series. With the component values shown the frequency can be varied over the approximate range 650Hz-7.2kHz via R2.

Fig 16 shows how the circuit can be further modified

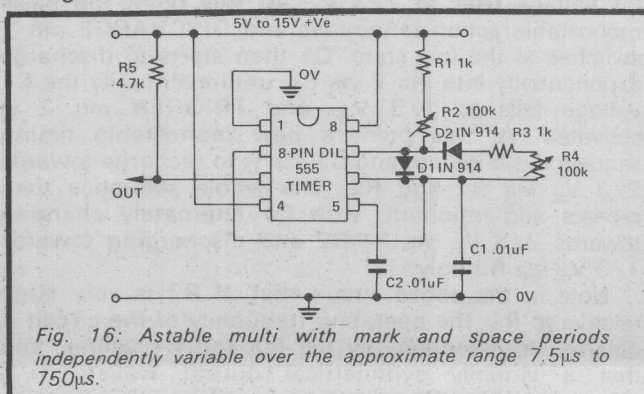

so that its MARK and SPACE periods are independently variable over the approximate range 7.5 μ s to 750 μ s. Here, timing capacitor C1 alternately charges via R1-R2-D1 and discharges via R3-R4-D2.

Fig 17 shows how the circuit can be additionally modified so that it acts as fixed-frequency square wave generator with a mark/space ratio or duty cycle that is fully variable from 1% to 99%. Here, C1 alternately

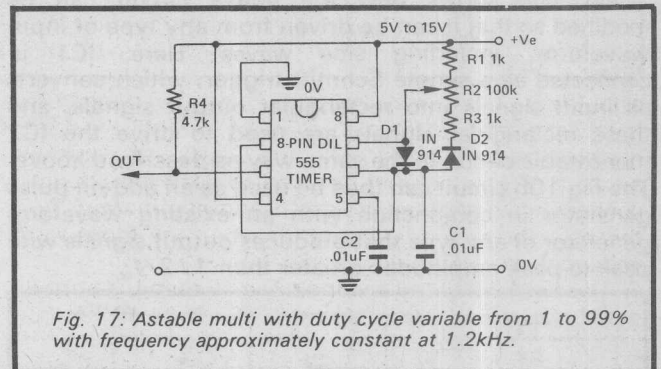


charges via R1 and the top half of R2 and via D1, and discharges via D2-R3 and the lower half of R2. Note that the sum of the two timing periods is virtually constant, so the operating frequency is almost independent of the setting of R2.

GATING A 555 ASTABLE

The 555 astable circuit can be gated ON or OFF, via either a switch or an electronic signal, in a variety of ways. Figs 18 and 19 show two basic ways of gating the IC via a switch.

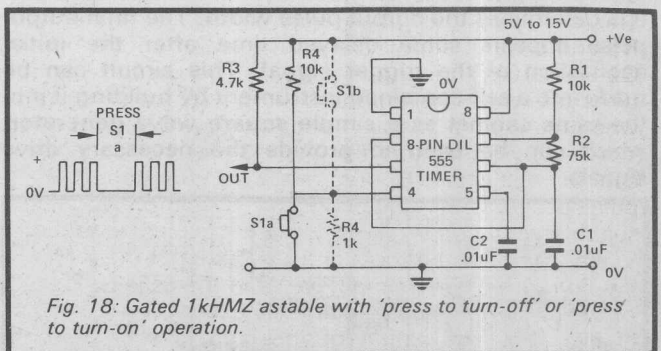In Fig 18 the circuit is gated via the pin 4 RESET



terminal. The characteristic of this terminal is such that, if the terminal is biased significantly above a nominal value of 0.7 volts, the astable is enabled, but if the terminal is biased below 0.7 volts by a current greater than 0.1mA (by taking the terminal to ground via a resistance less than 7k Ω , for example) the astable is disabled and its output is grounded. Thus, the Fig 18 circuit is normally on but can be turned off by closing S1 and shorting pin 4 to ground, while the circuit shown in dotted lines is normally gated off via R4 but can be turned on by closing S2 and shorting pin 4 to the positive supply rail. These circuits can alternatively be gated by applying suitable electronic signals directly to pin 4.

The Fig 19a and 19b circuits are gated via the pin 2 TRIGGER and pin 6 THRESHOLD terminals. The characteristic here is such that the circuit functions as a normal astable only as long as pin 6 is free to swing up to 2/3 V_{cc} and pin 2 is not biased below 1/3 V_{cc}. If these pins are simultaneously driven below 1/3 V_{cc} the

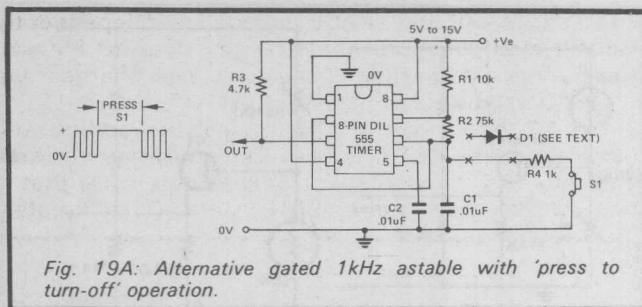


Fig. 19A: Alternative gated 1kHz astable with 'press to turn-off' operation.

astable action is immediately terminated and the output is driven to the high state. Thus, the Fig 19a circuit is normally on but turns off when S1 is closed. Note that an electronic signal can be used to gate the circuit by connecting a diode as indicated and eliminating S1. In this case the circuit will gate off when the input signal voltage is reduced below $1/3 V_{cc}$.

The Fig 19b circuit is connected so that it is normally gated off by saturated transistor Q1, but can be gated

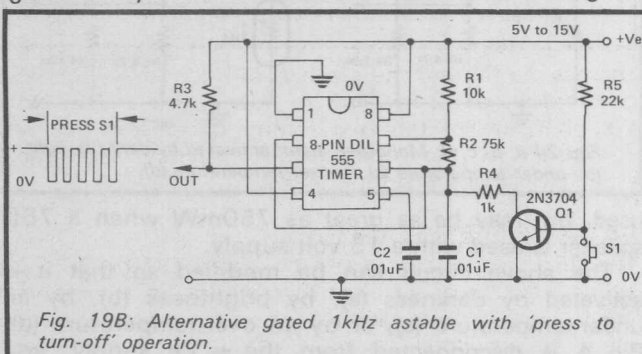


Fig. 19B: Alternative gated 1kHz astable with 'press to turn-off' operation.

on by closing S1 and thus turning the transistor off. This circuit can be gated electronically by eliminating R5 and S1 and applying a gating signal to the base of Q1 via a 10kΩ limiting resistor. In this case the astable turns off when the input signal is high, and turns on when the input signal is reduced below 0.7 volts or so.

All the 555 astable circuits that we have looked at can be subjected to frequency modulation (FM) or pulse-position modulation (PPM) by simply feeding a suitable modulation signal to pin 5. This modulation signal can take the form of an A.C. signal that is fed to pin 5 via a blocking capacitor, as in the case of Fig 20a or a D.C. signal that is fed directly to pin 5, as in the case of Fig 20b. The action of the chip is such that the voltage on pin 5 influences the width of the 'mark' pulses in each timing cycle, but has no influence on the 'space' pulses. Thus, since the signal on pin 5 influences the position of each 'mark' pulse in each timing cycle, this terminal provides pulse-position

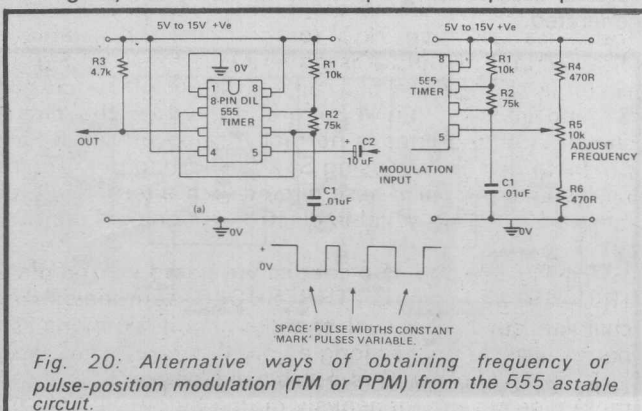


Fig. 20: Alternative ways of obtaining frequency or pulse-position modulation (FM or PPM) from the 555 astable circuit.

modulation (PPM), and, since the signal influences the total period of each cycle (and thus the frequency of the output signal), the terminal also provides frequency modulation (FM). These facilities are useful in special waveform generator applications, as is shown in the next section.

MISCELLANEOUS ASTABLE APPLICATIONS

The 555 astable multivibrator has three outstanding advantages over other types of astable circuit. First, its frequency can be varied over a wide range via a single resistive control. Second, its output has a low impedance and can source or sink current up to 200mA. Finally, its operating frequency can readily be modulated by applying a suitable signal to pin 5 of the IC. These features make the device exceptionally versatile, and it can be used in a vast range of practical applications of interest to both the amateur and professional user.

MORSE PRACTICE OSCILLATOR

Fig 21 shows how the 555 timer I.C. can be used as a morse-code practice oscillator. The circuit acts as a

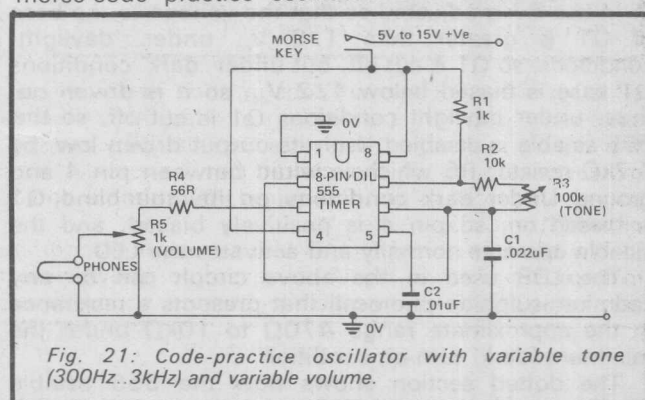


Fig. 21: Code-practice oscillator with variable tone (300Hz..3kHz) and variable volume.

normal astable, with frequency variable over the approximate range 300Hz — 3kHz via TONE control R3. The 'phone volume' is variable via R5, and the 'phones' can have any impedance from a few ohms up to megohms. The circuit draws zero quiescent current, since the normally-open morse key is used to connect the circuit to the positive supply rail, which can have any value in the range 5 volts to 15 volts.

Fig 22 shows how the 555 astable circuit can be used in LED flasher applications. This circuit operates at approximately 1 Hz, and has a single LED. The Fig 22 circuit has a single LED output; the dotted section shows how a second may be added, such that one LED is on while the other is off, and vice versa. Any types of LED's can be used in this circuit. Series resistors R₁ or

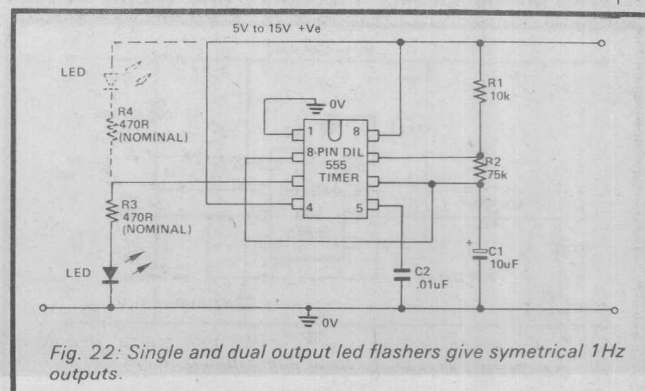


Fig. 22: Single and dual output led flashers give symmetrical 1Hz outputs.

555 TIMER APPLICATIONS

R_4 determines the ON current of each LED.

Fig 23 shows how the Fig 22 circuit can be modified to give automatic dark-activated operation. Here, R_4 and R_5 are wired as a fixed potential divider that sets $1/2 V_{cc}$ on the emitter of Q1, LDR and R_7 are wired as a light-sensitive potential divider that applies a variable voltage to the base of Q1, and the collector of Q1 is taken to RESET pin 4 of the IC, which is normally biased to ground via R_6 .

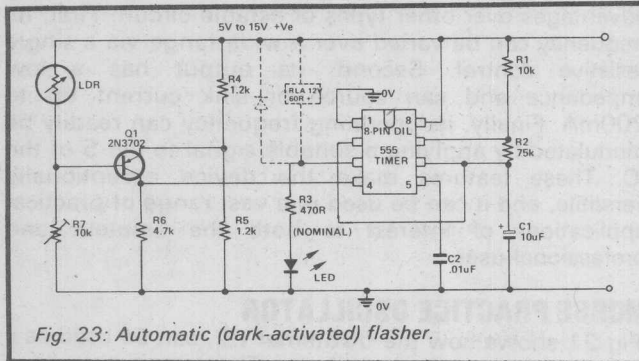


Fig. 23: Automatic (dark-activated) flasher.

In use R_7 is adjusted so that the voltage to the base of Q1 is greater than $1/2 V_{cc}$ under 'daylight' conditions, so Q1 is cut off, but under 'dark' conditions Q1 base is biased below $1/2 V_{cc}$, so it is driven on, thus, under daylight conditions Q1 is cut off, so the 555 astable is disabled, with its output driven low, by 4.7k resistor R_6 which is wired between pin 4 and ground. Under 'dark' conditions, on the other hand, Q1 is biased on, so pin 4 is positively biased, and the astable operates normally and activates the LED.

The LDR used in the above circuit can be any cadmium-sulphide photocell that presents a resistance in the approximate range 470 Ω to 10k Ω under the minimum 'dark' turn-on condition.

The dotted section shows how the 555 astable circuit can be used as a 12 volt relay pulser, which turns the relay on and off at a rate of one cycle per second. The relay can be any type with a coil resistance greater than 60 Ω .

ALARM GENERATOR

Fig 24 shows the connections for making an 800Hz monotone alarm-call generator. The circuit can be used with any supply in the range 5 to 15 volts, and with any speaker impedance. Note, however, that R_x must be wired in series with speakers having impedance less than 75 Ω , and must be chosen to give a total series impedance of at least 75 Ω , to keep the peak speaker currents within the 200mA driving constraints of the 555. The available alarm output power of the circuit depends on the speaker impedance and supply voltage

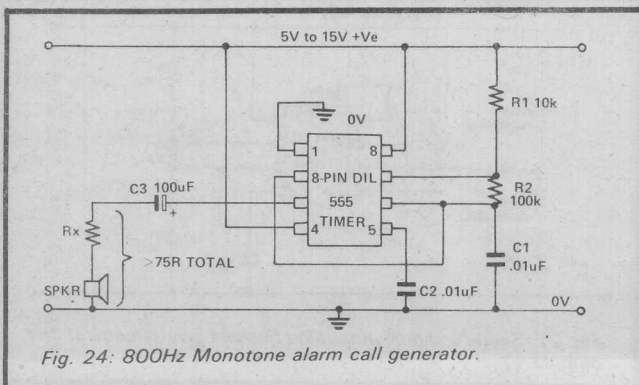


Fig. 24: 800Hz Monotone alarm call generator.

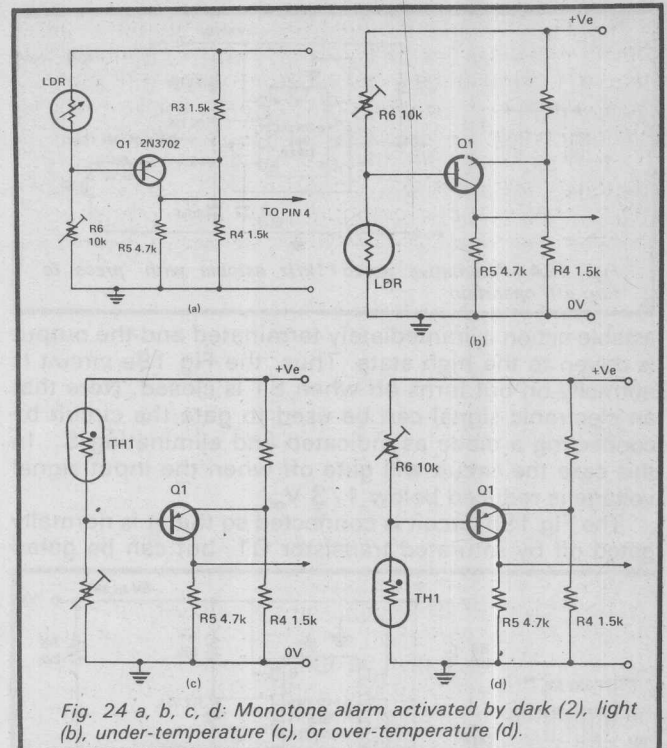


Fig. 24 a, b, c, d: Monotone alarm activated by dark (2), light (b), under-temperature (c), or over-temperature (d).

used, but may be as great as 750mW when a 75 Ω speaker is used with a 15 volt supply.

The above circuit can be modified so that it is activated by darkness (a), by brightness (b), by an under-temperature (c), or by an over-temperature (d). Pin 4 is disconnected from the + Ve supply, and connected to the triggering circuit, which is designed around Q1. This works in the same way as already described for the automatic (dark-activated) LED flasher. The LDR used in the light-activated versions of this circuit can be any cadmium-sulphide photocells that present resistances in the approximate range 470 Ω to 10k Ω at the desired turn-on levels. The thermistors used in the temperature-activated versions of the circuit can be any negative-temperature-coefficient types that present resistances in the same range at the required turn-on temperatures.

ALARMS AND SIRENS

The next 4 diagrams show a variety of useful alarm-call generator circuits. The Fig 25 circuit generates an 800Hz pulsed tone alarm call. Here, IC1 is wired as an 800Hz alarm generator, and IC2 is wired as a 1Hz astable which gates IC1 on and off via D1 once every second, thus causing a pulsed-tone output signal to be generated.



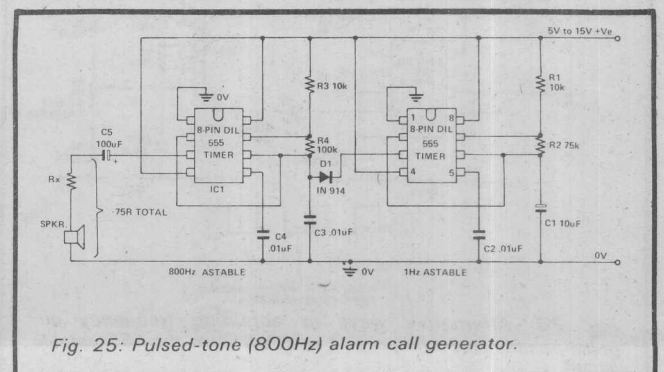


Fig. 25: Pulsed-tone (800Hz) alarm call generator.


The Fig 26 circuit generates a warble-tone alarm signal that simulates the sound of a British police siren. Here, IC1 is again wired as an alarm generator and IC2 is wired as a 1Hz astable multivibrator, but in this case the output of IC2 is used to frequency modulate IC1 via R5. The action is such that the output frequency of IC1 alternates symmetrically between 500Hz and 440Hz, taking one second to complete each alternating cycle.

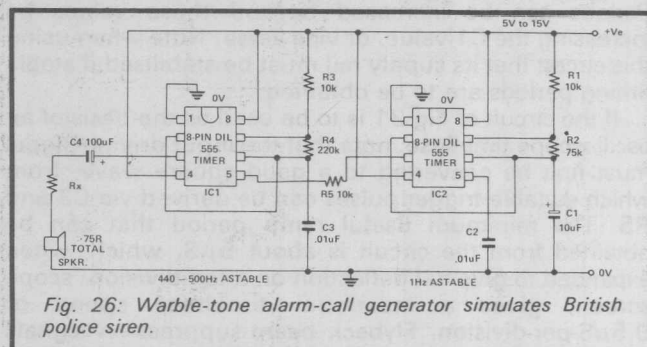

The circuit of Fig 27 generates a 'wailing' alarm that simulates the sound of an American police siren. Here, IC2 is wired as a low frequency astable that has a cycling period of about 6 seconds. The slowly varying 'ramp waveform on C₁ of this chip is fed to npn emitter follower Q1, and is then used to frequency modulate alarm generator IC1 via R6. IC1 has a natural centre frequency of about 800Hz. The circuit action is such that the alarm output signal starts at a low frequency, rises for 3 seconds to a high frequency, then falls over 3 seconds to a low frequency again, and so on add infinitum.

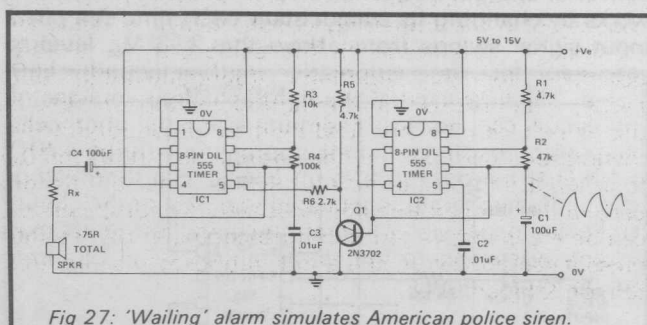

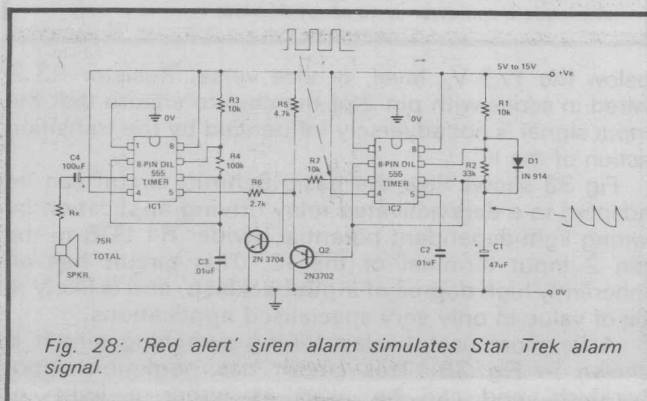Finally, to complete this quartet of alarm generator circuits, the Fig 28 circuit generates a siren alarm signal that is a simulation of the 'Red Alert' alarm used in the STAR TREK T.V. programme: This signal starts at a low frequency, rises for about 1.15 seconds to a high frequency, ceases for about 0.35 seconds, then starts




rising again from a low frequency, and so on add infinitum. The circuit action is as follows:

IC₂ is wired as a non-symmetrical astable multivibrator, in which C₁ alternately charges via R₁ and D₁, and discharges via R₂, thus giving a rapidly rising and slowly falling 'sawtooth' waveform across C₁. This waveform is fed to npn emitter follower Q₁, and is thence used to frequency modulate pin 5 of IC₁ via R₆. Now, the frequency modulation action of pin 5 of the IC₁ astable circuit is such that a rising voltage on pin 5 causes the astable frequency to fall, and vice versa; consequently the sawtooth modulation signal on pin 5 causes the astable frequency to rise slowly during the falling part of the sawtooth and collapse rapidly during the rising part of the sawtooth. The rectangular pin 3 output of IC₂ is used to gate IC₁ off via npn common emitter amplifier Q₂ during the collapsing part of the signal, so only the rising parts of the alarm signal are in fact heard, as in the case of the genuine STAR TREK 'Red Alert'.

MISCELLANEOUS APPLICATIONS

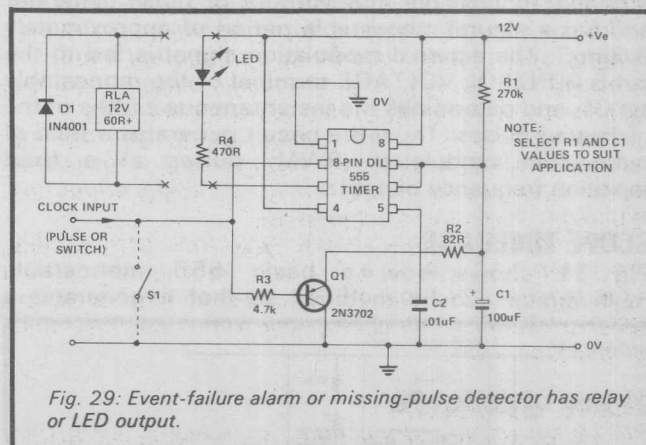To complete the 555 story, this final section shows a miscellany of 555 applications, of varying degrees of usefulness. Fig 29 shows how a single 555 can be used as the basis of an event-failure alarm or a missing-pulse detector, which closes a relay or illuminates an LED if a normally recurrent event fails to take place.



The operating theory of the circuit is fairly simple. The 555 is wired as a normal monostable pulse generator, except that transistor Q₁ is wired across timing capacitor C₁ and has its base taken to TRIGGER pin 2 of the IC via R₃. The TRIGGER pin is fed with a train of pulse- or switch-derived clock input signals from the monitored event, and the values of R₁ and C₁ are selected so that the monostable period of the IC is slightly longer than the repetition period of the clock input signal.


Thus, each time a clock pulse arrives, a monostable timing period is initiated via pin 2 of the IC, and C₁ is discharged and the pin 3 output is driven high via transistor Q₁. Before each monostable period can terminate, a new clock pulse arrives, and a new monostable period is initiated, so the pin 3 output terminal remains high so long as clock input pulses continue to arrive within the prescribed period limits. Should a clock pulse be missed, or the clock period exceed the pre-determined limits, however, the monostable period will be able to terminate normally, and pin 3 of the IC will go low and drive the relay or LED on. The circuit thus functions effectively as an

555 TIMER APPLICATIONS

event-failure alarm or missing-pulse detector. With the component values shown, the monostable has a natural period of about 30 seconds. This period can be varied via R1 and C4 to satisfy specific requirements.

Fig 30 shows how a couple of 555s can be used to make a pulse-width modulation (PWM) circuit. This circuit can be used for transmitting coded messages, or for applying variable power to a load at maximum efficiency.

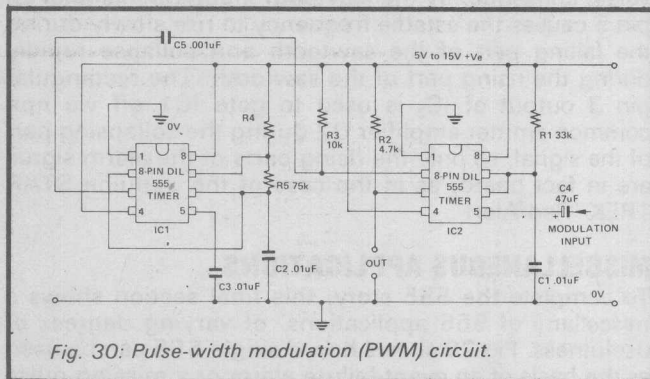
Here, IC1 is wired as a 1kHz astable multivibrator, which is used to feed a continuous train of clock pulses



to the pin 2 TRIGGER terminal of IC2, which is wired as a normal monostable multivibrator or pulse generator and has a natural monostable period of approximately 0.36mS. The external modulation signal is fed to the pin 5 CONTROL VOLTAGE terminal of the monostable via C4, and determines the instantaneous widths of the generated pulses. Thus, the circuit generates a train of pulse-width modulated (PWM) pulses at a fixed repetition frequency of 1kHz.

SCOPE TIMEBASE

Fig 31 shows how a basic 555 monostable multivibrator can be modified so that it generates a

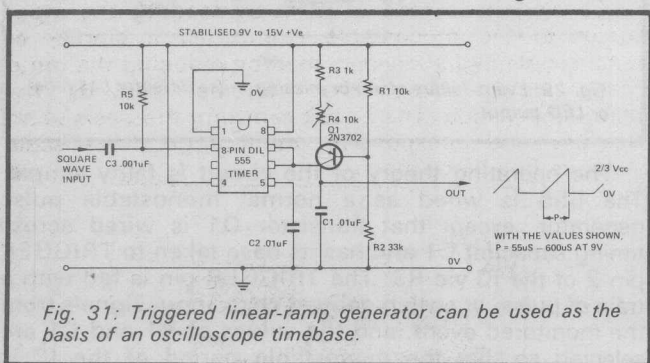

linear ramp waveform of fixed duration each time it is triggered. This circuit can form the basis of an excellent oscilloscope time-base generator. The circuit works just like a normal monostable circuit, except that timing capacitor C1 is charged via constant-current generator Q1 during each timing cycle, thus causing a linear ramp voltage to be generated across C1.

When a capacitor is charged via a constant-current generator, the voltage across the capacitor rises linearly at a predictable rate that is determined by the magnitudes of the charging current and the capacitance. The relationship can be expressed as:

Volts-per-second = I/C , when I is expressed in Amps and C is expressed in Farads.


In this circuit the charging current can be varied over

the approximate range 90µA to 1mA via R4, thus giving rates of rise on the 0.01µF capacitor of 9V-per-mS to 100V-per-mS. Now, remembering that each monostable period of the 555 circuit terminates at the point when C1 voltage reaches $2/3 V_{cc}$, and assuming that a 9V supply is used (giving a $2/3 V_{cc}$ value of 6V), it can be seen that the monostable cycles of the Fig 32 circuit have periods variable from 666µS to 60µS. Periods can be increased beyond these values by increasing the C1 value, or vice versa. Note when using this circuit that its supply rail must be stabilised if stable timing periods are to be obtained.

If the circuit of Fig 31 is to be used as the basis of an oscilloscope timebase, note that the input driving signal must first be converted to a good square wave, from which suitable trigger pulses can be derived via C3 and R5. The minimum useful ramp period that can be obtained from the circuit is about 5µS, which, when expanded to give full deflection on a ten-division 'scope screen, gives a maximum timebase speed of 0.5µS-per-division. Flyback beam-suppression signals can be derived from the pin 3 OUTPUT terminal of the IC.

The 'timebase' circuit gives superb signal synchronisation at trigger frequencies up to about 150kHz. If the timebase is to be used with input signal frequencies greater than this, the input signals should be divided down via a single- or multi-decade digital divider. Using this technique, the timebase can be used to view input signals up to many MHz.

Fig 32 shows how a 555 can be connected for use as a simple but effective Schmitt trigger or Sine/Square converter. The circuit acts as a good converter at input frequencies up to 150kHz or more. It works by changing its output state each time the pin 2 input signal swings from above the $2/3 V_{cc}$ level to

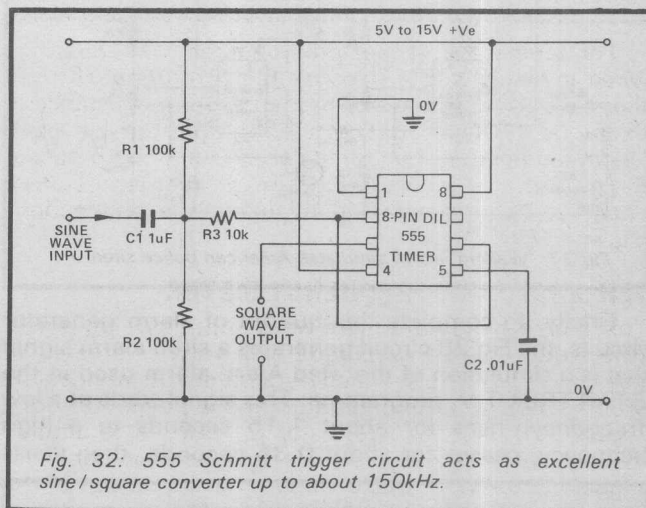

below the $1/3 V_{cc}$ level, or vice versa. Resistor R3 is wired in series with pin 2 of the chip to ensure that the input signal is not adversely influenced by the transition action of the IC.

Fig 33 shows how the basic Schmitt circuit can be adapted to a dark-activated relay driving application by wiring light-dependent potential divider R1-LDR to the pin 2 input terminal of the IC. This circuit has an inherently high degree of input backlash, and is likely to be of value in only very specialised applications.

A far more useful relay-driving switching circuit is shown in Fig 35. This circuit has negligible input backlash, and can be used as either a light- or

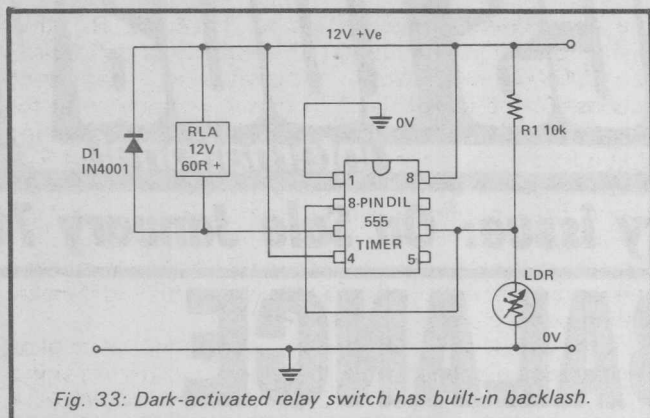


Fig. 33: Dark-activated relay switch has built-in backlash.

temperature-activated switch. In light-activated applications R1 is wired in series with a cadmium-sulphide photocell that presents a resistance in the approximate range 470Ω to 10kΩ at the required turn-on level. Dark-activated operation can be obtained by using the connections shown in Fig 34a or light-activated operation can be obtained by using the connections shown in Fig 34b.

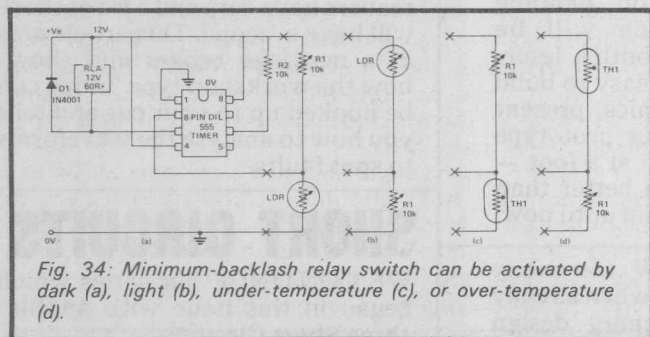


Fig. 34: Minimum-backlash relay switch can be activated by dark (a), light (b), under-temperature (c), or over-temperature (d).

For temperature-activated operation, R1 must be wired in series with a negative-temperature-coefficient thermistor. This thermistor must present a resistance in the range 470Ω to 10kΩ at the required turn-on level. Under-temperature operation can be obtained by using the connections shown in Fig 34c, or over-temperature operation can be obtained by using the connections shown in Fig 34d.

1kHz ANALOGUE FREQUENCY METER

This circuit needs a square-wave input driving signal with a peak-to-peak amplitude of 2 volts or greater. In this circuit the 555 is wired as a standard monostable multivibrator or pulse generator, and is powered from a regulated 6V supply. Transistor Q1 is used to amplify the square wave input signals to a level suitable for triggering the monostable stage, and the output of the monostable is fed to 1mA f.s.d meter M1 via multiplier resistor R5 and offset-cancelling diode D1. This meter gives a reading that is directly proportional to the frequency of the square wave input signals, and its operating theory is as follows:

Each time the monostable multivibrator is triggered it generates a pulse of fixed duration and fixed amplitude. If we assume that each generated pulse has a peak amplitude of 10V and a period of 1mS, and that the pulse generator is triggered at an input frequency of 500Hz, it can be seen that the pulse is high (at 10V) for 500mS in each 1000mS (one second) total period, and that the MEAN value of output voltage measured over this total period is $250\text{mS}/1000\text{mS} \times 10\text{V} = 5\text{V}$, or

50% of 10V. Similarly, if the input frequency is 250Hz the pulse is high for 250mS in each 1000mS total period, so the mean output voltage equals $250\text{mS}/1000\text{mS} \times 10\text{V} = 2.5\text{V}$, or 25% of 10V. Thus, the mean value of output voltage of the pulse generator, measured over a reasonable total number of pulses, is directly proportional to the repetition frequency of the generator.

Normal moving coil meters are 'mean' reading instruments, and in the Fig 35 circuit a 1mA f.s.d. moving coil meter is wired in series with voltage multiplier resistor R5, which sets the meter sensitivity at about 3.4V f.s.d, and is connected so that it reads the

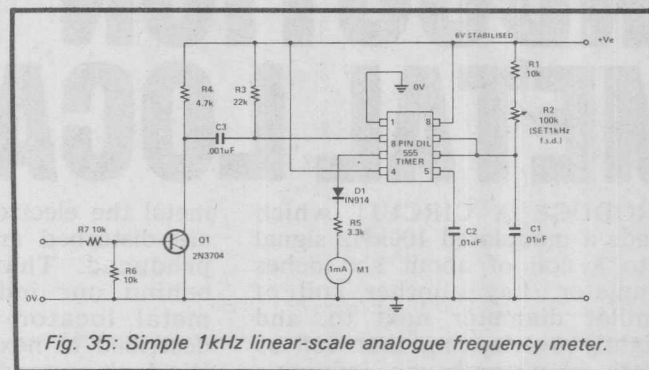


Fig. 35: Simple 1kHz linear-scale analogue frequency meter.

mean output voltage of the pulse generator. This meter thus gives a reading that is directly proportional to frequency, and the circuit thus acts as a linear-scale analogue frequency meter. With the component values shown the circuit is intended to read f.s.d at 1kHz. To set up the circuit initially, simply feed a 1kHz square wave signal to its input, and then adjust R2 (which controls the pulse lengths) to give full-scale reading on the meter; all adjustments are then complete.

The full-scale frequency of the above circuit can be varied from about 100Hz to about 100kHz by suitable choice of C1 value. The circuit can be used to read frequencies up to tens of MHz by feeding the input signals to the monostable circuit via a single- or multi-decade digital divider, thereby reducing the input frequencies to values that can be read by the monostable circuit. The circuit can form the basis of an excellent and inexpensive multi-range linear-scale analogue frequency meter.



"Do you think we should bring in the generating boys before we hit the market with these."

electronics today

international

What to look for in the February issue: On Sale January 7th

INDUCTION BALANCE METAL LOCATOR

PRODUCE A CIRCUIT which feeds a modulated 100kHz signal into a coil of about six inches diameter. Lay another coil of similar diameter next to, and slightly overlapping that coil so there is virtually no inductive pick-up. Amplify greatly the small signal that is picked up but gate it so that an audio amplifier will just not produce an output.

When the coils are brought near

metal the electro-magnetic fields are disturbed and an output is produced. That's the theory behind our induction balance metal locator which will be described in next month's issue. We don't pretend it's easy to build (though the electronics present few problems) but our prototype will sniff out a 2p coin at a foot — and that's very much better than any design published up until now!

YAMAHA B-1 AMPLIFIER



WE DON'T REVIEW too many amplifiers in ETI, but when a really interesting, revolutionary design comes along we know you want to hear about it. The Yamaha B1 Vertical FET Power Amplifier comes into this category. It gives over 200W with a performance that stretches your measuring equipment to the limit. We also explain the principle of operation in detail.

Computers for small Businesses

MINICOMPUTERS continue to fall in price and increase in performance. Once the exclusive companion of the large corporation, computers are now finding their way into smaller and smaller companies, reducing drudgery and improving efficiency (when properly used). The day will soon be with us when any company big enough to have a telephone switchboard will boast its own computer.



'Scope Test your Car


A HIGH PROPORTION of ETI readers have cars and a lot of those will have a 'scope. This article acts as a marriage broker and shows how the workshop type 'scope can be hooked up to your car and tells you how to analyse the waveforms to spot faults.

SHORT CIRCUITS

WE CONTINUE our series which began in this issue with another three Short Circuits:

1. **Test-bench Amplifier.** Useful by itself but ours has been modified simply to act as an audio millivoltmeter as well.
2. **LED Dice Unit.** An electronic dice using only two ICs and six inexpensive LED's.
3. **Two Tone Doorbell.** Another straightforward project for the home — this time using a 555.

DISCO MIXER

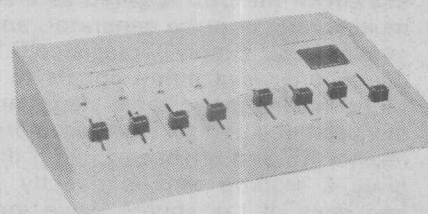

This article describes a general purpose mixer which can be tailored by the reader to meet a specific application. Prefade 'listen' is included as a facility and allowance is even made for balanced inputs.

The articles described here are in an advanced state of preparation but circumstances may necessitate changes in the issue that appears.